

# **Ultra-Low Power PLL for Wake-up Receiver Applications**

**Specialization Project Progress - 5th Week**

Cole Nielsen

Department of Electronic Systems, NTNU

27 September 2019 (Week 39)

# Autumn Timeline

Week Number	Dates	Tasks	Outcomes
36	2.9 - 8.9	Review PLL Design	Refreshed Knowledge
37	9.9 - 15.9	Modeling/simulation (set up)	–
38	16.9 - 22.9	Modeling/simulation	TDC/DCO Requirements
39	23.9 - 29.9	Modeling/simulation	Loop Filter/Digital Algorithms
40	30.9 - 6.10	Modeling/simulation	<b>Loop filter</b> , Ideal implementation in Cadence
41	7.10 - 13.10	Circuit Research	DCO/Divider topologies
42	14.10 - 20.10	Circuit Research	TDC/other topologies
43	21.10 - 27.10	Circuit Implementation	Digital logic (schematic)
44	28.10 - 3.11	Circuit Implementation	DCO (schematic)
45	4.11 - 10.11	Circuit Implementation	Divider/other (schematic)
46	11.11 - 17.11	Circuit Implementation (TDC)	
47	18.11 - 24.11	Circuit Implementation (TDC)	TDC (schematic)
48	25.11 - 1.12	Full Circuit testing	Testbenches, find bugs, design fixes
49	2.12 - 8.12	Full Circuit testing	Design Fixes/iteration
50	9.12 - 15.12	–	–

Legend: Done Current Revised

# Timeline Tasks

## This week



- **Primary:** Loop analysis, requirements definition.
  - Design open loop filter design to meet closed loop requirements.
    - Dependent on DCO properties ( $k_{DCO}$ ,  $f_0$ , tuning range).
    - Difference equation implementing discrete time 2nd order IIR filter.
  - Datapath requirements (fixed-point resolution)

## Next week - Revised

- **Primary:** Ideal component PLL implementation in Cadence, **continue loop filter work.**
  - Ideal component PLL implementation is not a lot of work.
  - Loop filter very critical, spend more time on this.
    - Need to make Verilog description of loop filter for simulation in Cadence.

# Loop Filter

## Original Attempt

  


- Started with simple PLL loop with proportional-phase fed into loop filter (LF).
  - Not stable at large frequency offset, due to frequency wrapping. At the TDC:

$$\Delta\phi = \frac{2\pi\Delta f T}{N} \rightarrow T_{wrap} = \frac{N}{\Delta f} \quad (1)$$

- Upon cold start,  $\Delta f$  is expected to be up to 100 MHz,  $N=150 \rightarrow T_{wrap} = 1.5 \mu s$ 
  - $f_{wrap} \sim 600$  kHz, this is unstable with a loop bandwidth of 100 kHz.
- Must opt for alternate loop structure.

# Loop Filter


## New Approach

 

- Two-fold approach: utilize proportional-phase and coarse frequency offset estimation in feedback.
  - Coarse frequency estimator to handle high frequency offset (e.g. cold start-up).
  - Proportional-phase for near steady state. Acts like fine frequency estimator.
- Offset estimates are summed with previous oscillator tuning word (OTW, also  $f_{ctrl}$  here), then low passed filtered to yield new OTW.
  - Low pass filter loop keeps steady state.

# Loop Filter

## Coarse frequency offset estimation

 

- **Coarse frequency estimation:** Given M-step TDC, outputting phase error signal  $e_\phi[n]$ , and a divider modulus N

$$\Delta\phi_{DCO}[n; q] = N \cdot \Delta\phi_{REF}[n] = 2\pi \frac{N}{M} (e_\phi[n] - e_\phi[n - q]) , \quad \Delta\phi_{DCO}[n; q] = \Delta\omega_{DCO}[n]qT_{ref} = 2\pi q \frac{\Delta\tilde{f}_{DCO}}{f_{ref}} \quad (2)$$

$$\Delta\tilde{f}_c = \Delta\tilde{f}_{DCO} = \frac{f_{ref}}{q} \frac{N}{M} (e_\phi[n] - e_\phi[n - q]) \quad (3)$$

- Is a discrete differentiator, with gain coefficient to convert  $d\phi/dt$  to frequency.
  - Design logic to handle phase wrapping.
  - Useful in coarse frequency range calibration. Can detect fast if frequency offset too large.
  - Delay  $q$  is used to increase frequency resolution.

# Loop Filter

## Coarse frequency offset estimation - continued

- Given DCO gain  $K_{DCO}$ , the required gain  $K_d$  of the filter is:

$$K_d = \frac{f_{ref}}{qK_{DCO}} \frac{N}{M} (e_\phi[n] - e_\phi[n - q]) \quad (4)$$


- Disable the coarse estimator if  $e_\phi[n] - e_\phi[n - q] < \text{some threshold}$ :
  - Offset small enough, allow to run as classical phase-detector mode.

## Fine frequency offset estimation

- Proportional signal of phase error to estimate frequency error.
- Used in near-steady state. Loop will regulate to keep phase locked.
- Classical PLL operating mode.

# Loop Filter

## Loop Filter Gain Coefficients

 

- When running in proportional-only feedback mode, the open loop gain  $A(f)$  is:

$$A(f) = K_p \frac{M}{N} \frac{K_{LPF}}{s + \omega_{LPF} - K_{LPF}} \frac{2\pi K_{DCO}}{s} \quad (5)$$

- The closed loop gain is therefore (continuous):

$$G(f) = \frac{A(f)}{1 + A(f)} = \frac{2\pi MK_p K_{LPF} K_{DCO} / N}{s^2 + s(\omega_{LPF} - K_{LPF}) / N + 2\pi MK_p K_{LPF} K_{DCO} / N} \quad (6)$$



# Loop Filter

## Loop Filter Gain Coefficients

- The form of a second order low pass filter is, with natural frequency  $\omega_n$  and damping coefficient  $\zeta$ :

$$H_{LPF}(f) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} \quad (7)$$

- Setting  $H_{LPF}(f) = G(f)$ , equivalencies for  $\omega_n$  and  $\zeta$  are found:

$$\omega_n = \sqrt{2\pi M K_p K_{LPF} K_{DCO} / N} \quad (8)$$

$$\zeta = \frac{\omega_{LPF} - K_{LPF}}{2\sqrt{2\pi M N K_p K_{LPF} K_{DCO}}} \quad (9)$$

- The Butterworth closed loop response with 100 kHz bandwidth,  $\omega_n \sim 2\pi \cdot 100\text{Khz}$ ,  $\zeta = 0.707$ .
- Coefficients  $K_{LPF}$ ,  $K_p$ ,  $\omega_n$  can be solved computationally.
- Need to reformulate in Z-domain.

# Frequency Calibration

## Coarse frequency calibration algorithm

- Ring oscillator DCOs will have large variation in frequency due to PVT variation.
- Use bank of coarse capacitance values to correct range of oscillator.
- Coarse frequency estimator used in this calibration. DCO is has a fine range of  $\Delta f_{fine}$ .

### Coarse frequency tuning state machine (as pseudo-code)

1.  $C_{tune} = C_{opt} = 0$ ;  $LE = \Delta f_{fine}$
2. Reset PLL
3. Estimate Frequency offset  $\rightarrow \tilde{f}_{offset}$
4. **If**  $\text{abs}(\tilde{f}_{offset} - \Delta f_{fine}/2) < LE$ : *// Centers fine tuning range around target frequency*
  - $LE = \text{abs}(\tilde{f}_{offset} - \Delta f_{fine}/2)$
  - $C_{opt} = C_{tune}$
5. **If**  $C_{tune} == C_{max}$ : **Goto** 8
6.  $C_{tune} += 1$
7. **Goto** 2
8.  $C_{tune} = C_{opt}$ ; **End**

# Specification (unchanged)

## System Performance Targets

Parameter	Value	Unit	Notes
Frequency	2.4-2.4835	GHz	2.4G ISM Band
Ref. frequency	16	MHz	Yields 6 channels
Power	$\leq 100$	$\mu\text{W}$	
Residual FM	$\leq 107$	$\text{kHz}_{RMS}$	$\text{BER} \leq 1\text{e-}2$ , $f_{dev} = \pm 250 \text{ KHz}$
Initial Lock Time	$\leq 50$	$\mu\text{s}$	Upon cold start
Re-lock Time	$\leq 5$	$\mu\text{s}$	Coming out of standby
Bandwidth	100	kHz	(nominally), tunable

Additionally: PLL output should support IQ sampling at LO frequency.


# Specification (new)

## PLL Component Performance Targets

Parameter	Value	Unit	Notes
DCO LSB Resolution	$\leq 50$	kHz	Determined from quantization noise.
DCO DNL	$< 1$	LSB	Ensures monotonicity
TDC Resolution	$\leq 3.8$	ns	
TDC Resolution (bits)	$\geq 4.03$	bits	

# Architecture (unchanged)

## Block Diagram

 

## Power Targets

DCO	TDC	Divider	Other	SUM
70 $\mu$ W	20 $\mu$ W	10 $\mu$ W	$\ll 1$ $\mu$ W	100 $\mu$ W

# Project Phases

## Autumn 2019

- System modeling and simulation.
  - Learn PLL theory in detail
  - Evaluate feasibility of PLL architectures (counter, TDC-based)
  - Determine requirements for TDC/DCO/Divider/logic (bits of resolution, accuracy etc) to meet PLL performance specifications.
  - Determine digital logic for loop filter, validate stability and lock time performance.
- Research ultra-low power circuit topologies to implement system components that will meet determined requirements.
- Translate component-level specifications into schematic-level circuit designs.
  - Try, fail, try again until functional at schematic level.
    - I expect the TDC to be difficult.

# Project Phases (continued)

## Spring 2020

- Finalize schematic-level design.
- Establish thorough tests for PLL performance (automated?) to help in layout.
- Layout of PLL.
  - Design iteration until design specs met.
  - Probably very time consuming.
- Full characterization/validation of design performance.
  - Comprehensive Corners/Monte-Carlo testing (time consuming??)
  - More design iteration if new issues crop up...
- Thesis paper writing.